

www.MINEPORTAL.in

(All Mining Solutions)

DOWNLOAD MINEPORTAL APP FROM GOOGLE PLAY STORE

- **ONLINE TEST SERIES FOR**
 - DGMS COAL/METAL FIRST & SECOND CLASS
 - GATE MINING
 - COAL INDIA EXAMS
 - OTHER PSUs MINING EXAMS
- **FREE STUDY MATERIAL-MINEPORTAL NOTES & USER NOTES**
- **MINING VIDEO LECTURES**
- **DISCUSSION FORUM**
- **WHATSAPP CHAT SUPPORT FOR MINING EXAMS & QUERY RELATED TO MINING**

CALL/WHATSAPP- 8804777500

VISITING SITE- www.MINEPORTAL.in

Facebook- www.fb.com/mineportal.in

EMAIL- INFO@MINEPORTAL.IN



IIT(BHU) VARANASI
STUDENTS' NOTES
TOPIC-ELECTRICAL-II

www.MINEPORTAL.in

$$\begin{aligned}
 -v_3)2 + 6 + (v_1 - v_3)x4 - v_3x \\
 = 0 \\
 +8 + 4v_1 - 4v_3 - 5v_3 = 0 \\
 v_2 - 11v_3 = -6 \quad \text{--- (3)} \\
 v_2 = -\frac{326}{439}, \quad v_3 = \frac{254}{439}
 \end{aligned}$$


4/02/2013

Teacher - II

Determination of Eq't. Ckt. parameters

Open Circuit test

(Conducted from low voltage side)

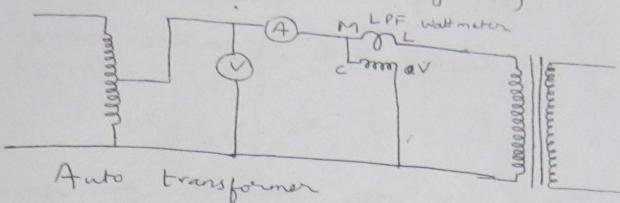


V = V_{rated} voltage

I = around 5% of full load current.

W_0 = no load power, W_0 .

Equivalent circuit

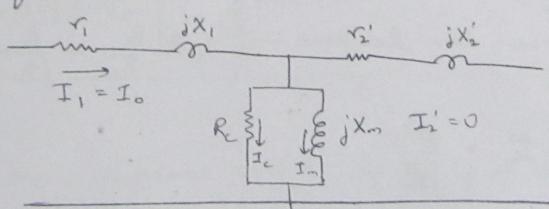

Core loss, $P_0 = W_0 - I_0^2 r_1$

No load power factor, $\cos \phi_0 = \frac{P_0}{V_0 I_0}$

No load current has two components,
 I_c and I_m .

$$\bar{I}_0 = \bar{I}_c + \bar{I}_m$$

I_c is active current or

$$I_c = I_o \cos \phi_o \quad (\text{active current})$$

$$\text{and } I_m = I_o \sin \phi_o \quad (\text{reactive current})$$

$$\bar{E}_1 = \bar{V}_o - I_o (r_1 + jx_1)$$

If $r_1 + x_1$ are unknown, then ignore
 $I_o^2 r_1 + I_o (r_1 + jx_1)$

$$\bar{E}_1 \approx \bar{V}_o$$

$$\text{or } P_o = W_o$$

$$\text{so Core loss} = I_c^2 R_c = P_o$$

$$\text{Core loss resistance} - R_c = \frac{P_o}{I_c^2} = \frac{P_o}{(I_o \cos \phi_o)^2}$$

$$\bar{I}_m = \frac{\bar{E}_1}{jx_m}$$

$$\text{Magnetizing Reactance, } X_m = \frac{E_L}{I_m} = \frac{E_L}{I_o \sin \phi_o}$$

Q. In a 110V/220V 50Hz, 1.5 kVA true winding transformer, the open circuit test gives, $V_o = 110V$, $I_o = 0.8 \text{ Amp}$, $W_o = 18 \text{ W}$

$$\begin{aligned} R_c &= ? \\ X_m &= ? \\ \cos \phi_o &= ? \end{aligned} \quad \left| \begin{array}{l} I_c = ? \\ I_m = ? \end{array} \right. \quad \left| \begin{array}{l} V_o = 110V \\ I_o = 0.8 \text{ A} \end{array} \right.$$

$$\cos \phi_o = \frac{18}{110 \times 0.8} = 0.2045$$

$$\sin \phi_o = 0.958$$

$$I_c = I_o \cos \phi_o = 0.8 \times 0.2045 = 0.1636 \text{ A}$$


$$I_m = I_o \sin \phi_o = 0.8 \times 0.958 = 0.7664 \text{ A}$$

$$R_c = \frac{P_o}{I_c^2} = \frac{18}{(0.1636)^2} = 703 \Omega$$

$$X_m = \frac{E_L}{I_m} = \frac{110}{0.7664} = 144 \Omega$$

Short Circuit Test

(performed from high voltage side).

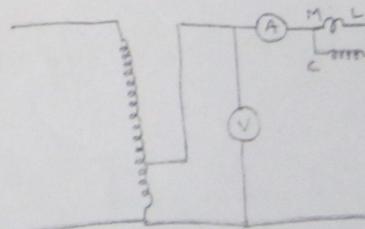

I_{sc} = Rated current

V_{sc} = (low voltage)

w_{sc} = (Rating of primary coil)

current or
 (active current)
 (reactive current).

$$I_o (r_i + jx_i)$$

unknown, then ignore
 $(r_i + jx_i)$

$$I_e^2 R_c = P_o$$

$$R_c = \frac{P_o}{I_e^2} = \frac{P_o}{(I_o \cos \phi)^2}$$

$$L_o = \frac{E_1}{I_m} = \frac{E_1}{I_o \sin \phi}$$

fxVA true

open circuit

$$I_o = 0.8 \text{ Amp., } W_o = 18 \text{ W}$$

$$\begin{aligned} X_m &= ? \\ \cos \phi_o &= \end{aligned}$$

$$I_m =$$

Wattmeter
ammeter
voltmeter
voltmeters measure
of turns with same

$$\cos \phi_o = \frac{18}{110 \times 0.8} = 0.2045$$

$$\sin \phi_o = 0.958$$

$$I_c = I_o \cos \phi_o = 0.8 \times 0.2045 = 0.16 \text{ Amp.}$$


$$I_m = I_o \sin \phi_o = 0.8 \times 0.958 = 0.76 \text{ Amp}$$

$$R_c = \frac{P_o}{I_e^2} = \frac{18}{(0.16)^2} = 703 \Omega$$

$$X_m = \frac{E_1}{I_m} = \frac{110}{0.76} = 144.7 \Omega$$

Short Circuit Test

(performed from high voltage side).

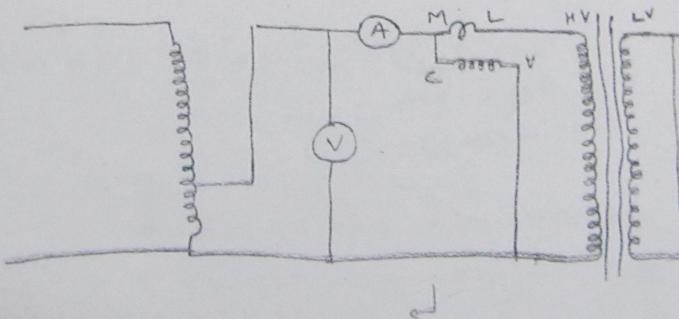


I_{sc} = Rated current

V_{sc} = (low voltage)

w_{sc} = (Rated Efficiency, 100%)

Cores losses are assumed to be zero.

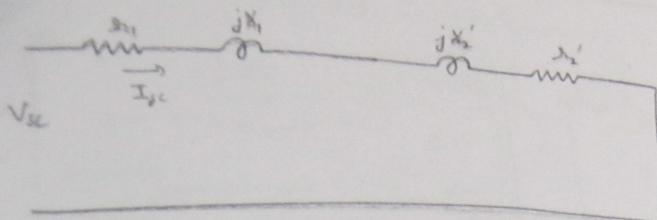

$$\text{Short circuit power factor}, \cos \phi_a = \frac{W_{sc}}{V_{sc} \cdot I_{sc}}$$

$$\text{Copper loss} \approx \text{active loss}, W_{sc} = (r_1 + r_2') I_{sc}^2$$

$$r_1 + r_2' = \left(\frac{W_{sc}}{I_{sc}^2} \right)$$

If r_1 is known,
 r_2' is known also ($r_1 + r_2'$).

$$\overline{I_{sc}} = I_{sc} \cos \phi_{sc} + j I_{sc} \sin \phi_{sc}$$

$$\text{Impedance of circuit}, Z = \frac{V_{sc}}{\overline{I_{sc}}} = (r_1 + r_2') + j(X_1 + X_2')$$

$$= \sqrt{(r_1 + r_2')^2 + (X_1 + X_2')^2}$$

$$(X_1 + X_2') = \left(\frac{V_{sc}}{I_{sc}} \right)^2 - \left(\frac{W_{sc}}{I_{sc}^2} \right)$$

$$X_1 \approx X_2'$$

Q. In a short ckt test, $I_{sc} = 6$
& $V_{sc} = 25 \text{ V}$, $W_{sc} = 150 \text{ W}$. Calculate
 $r_1 + r_2'$, $X_1 + X_2'$.

$$\cos \phi_{sc} = \frac{150/150}{25 \times 6.8} = 0.88$$


$$(X_1 + X_2') = \left(\frac{25}{6.8} \right)^2 - \left(\frac{150}{6.8} \right)^2$$

$$= 13.51 - 3.24$$

$$= 10.26$$

$$Z = \frac{25}{6.8} = 3.676 = \sqrt{(r_1 + r_2')^2}$$

Equivalent ext. ref. to high

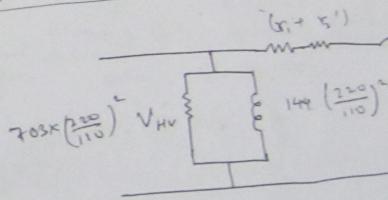

& Find the referred values of
Re. ref. to HV

$$X_m \text{ ref. to HV } X_m |_{HV}$$

Q. In a short circuit test, $I_{sc} = 6.8 \text{ Amp}$, $V_{sc} = 25 \text{ V}$, $W_{sc} = 150 \text{ W}$. Calculate, $r_1 + r_2'$, $X_1 + X_2'$.

$$\cos \phi_{sc} = \frac{150}{25 \times 6.8} = 0.88$$


$$(X_1 + X_2') = \left(\frac{125}{6.8} \right)^2 - \left(\frac{150}{6.8} \right)^2$$

$$Z = \frac{25}{6.8} = 3.676 = \sqrt{(r_1 + r_2')^2 + (X_1 + X_2')^2}$$

$$= 10.26$$

$$\approx 13.51 = 3.24$$

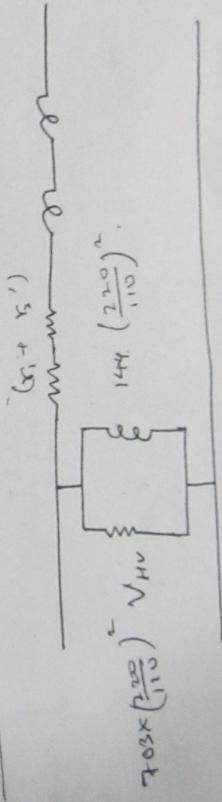Equivalent ckt. ref. to high voltage side



a. Find the referred values of R_c from HV side.

$$R_c \text{ ref. to HV} \quad R_c|_{HV} = R_c|_{LV} \cdot a^2$$



$$= 703 \times \left(\frac{220}{110} \right)^2$$

$$X_m \text{ ref. to HV} \quad X_m|_{HV} = X_m|_{LV} \cdot a^2 = 144 \times \left(\frac{220}{110} \right)^2$$

(Any book dealing with transformer
 (Electrical Machines)
 (Nagrath & Kotwali).

05/10/2013

Teacher - I

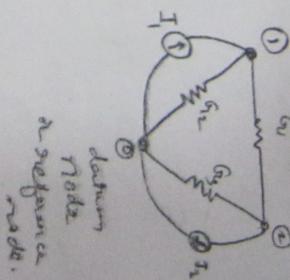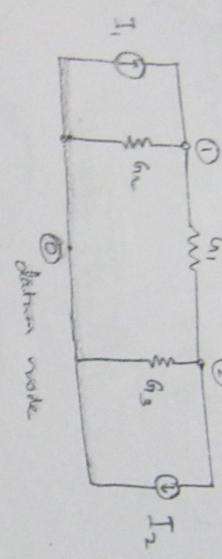

KCL at node ① } Current entering node ① = sum of currents leaving node ①

$$\therefore I_1 = V_1 \delta_{12} + (V_1 - V_2) \delta_1$$

KCL at node ② } Current entering node ② = sum of currents leaving node ②

$$= I_2 = V_2 \delta_{12} + (V_2 - V_1) \delta_2$$

$$\begin{bmatrix} I_1 \\ -I_2 \end{bmatrix} = \begin{bmatrix} G_{11} + G_{22} & -G_{12} \\ -G_{21} & G_1 + G_2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

A

© 11/02/2013

order


$$\text{Based on second der of } \Delta = \begin{bmatrix} 7+14 & -6+5 \\ -6+3+14 & 1 \end{bmatrix} = \begin{bmatrix} 21 & -1 \\ -3 & 1 \end{bmatrix}$$

$$3+1+2=6$$

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -4 \\ -2 \\ -2 \end{bmatrix}$$

G_1 node
admin node
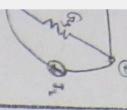
$$G_1^{-1} I = G_1^{-1} G_1 \quad \checkmark$$



$$G_1^{-1} I = V$$

return
node
efficiency
node.

Graver's rule

$$V_1 = \begin{pmatrix} -5 & -3 & -4 \\ -7 & 6 & -2 \\ 6 & -2 & 11 \end{pmatrix}$$

if leaving
node \checkmark

G_1

$$V_1 = \frac{5 \left(\frac{6^2}{2} \right) + 3(-77 + 12) - 4(14 - 34)}{11(66 + 4) + 3(-33 - 8) - 4(8 + 24)}$$

if leaving
node \checkmark

G_1

$$V_1 = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix}$$

$$= \frac{350 + -195 + 488}{770 - 123 - 120}$$

$$= \frac{203}{547 - 243} = 0.4024$$

$$V_2 = \frac{-32.6}{403.9} = -0.743V$$

$$V_3 = \frac{1}{R} = \frac{\begin{vmatrix} 4 & -3 & 5 \\ -3 & 6 & -7 \\ -2 & -2 & 6 \end{vmatrix}}{403.9} = \frac{259}{403.9} = 0.571$$

Conductance


$$G = \frac{1}{R}$$

$$Y = \frac{1}{R T j X} \text{ impedance}$$

↙
admittance.

0.81/0.92/2

0.81/0.92/2

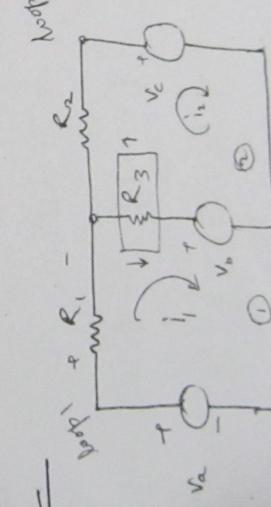

KVL

loop ① : $V_d + R_1 i_1 - R_2 i_2 = 0$

$$\text{KVL } ① : V_d - R_3 (i_1 - i_2) - R_2 i_2 - V_a = 0$$

$$\text{KVL } ② : V_d - R_3 (i_1 - i_2) - R_2 i_2 - V_a = 0$$

$$-R_1 i_1 - R_3 (i_1 - i_2) = V_b - V_a$$

$$R_3 (i_2 - i_1) + R_2 i_2 = V_b - V_c \quad \text{---(1)}$$

$$+ R_1 i_1 + R_3 (i_1 - i_2) = V_a - V_b \quad \text{---(2)}$$

$$\begin{bmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_a - V_b \\ V_b - V_c \end{bmatrix}$$


loop impedance matrix

$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_a - V_b \\ V_b - V_c \end{bmatrix}$$

08/02/2013

Clinical Test - I of Electrical
 Date : 19-02-2013 Tuesday
 Time : 08:00 am to 09:00 am,
 Venue : Survey Hall.

Teacher-T

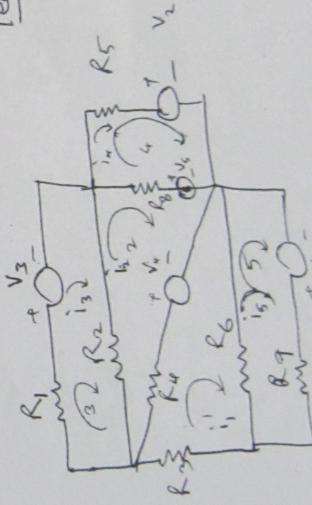


08/02/2013

$$V_{n \times 1} = Z_{n \times n} I_{n \times 1}$$

$$\begin{bmatrix} -V_4 \\ V_4 - V_5 \\ -V_3 \\ V_5 - V_2 \\ \text{--- } V_1 \end{bmatrix} = \begin{bmatrix} R_3 + R_4 + R_6 \\ . \\ . \\ . \\ . \end{bmatrix} \quad \text{Date: 12/02/2013}$$

$$\begin{bmatrix} a_{11} & a_{12} & a_{13} & a_{14} & a_{15} \\ a_{21} & a_{22} & a_{23} & a_{24} & a_{25} \\ a_{31} & a_{32} & a_{33} & a_{34} & a_{35} \\ a_{41} & a_{42} & a_{43} & a_{44} & a_{45} \\ a_{51} & a_{52} & a_{53} & a_{54} & a_{55} \end{bmatrix}$$
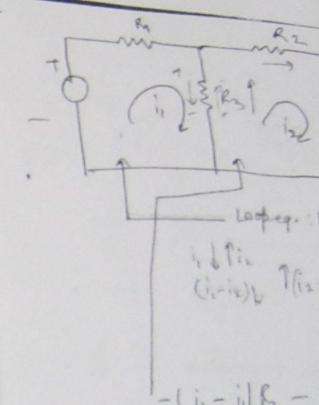
$$Z \begin{bmatrix} R_3 + R_4 + R_6 & R_4 & 0 & 0 & -R_6 \\ -R_4 & R_2 + R_4 + R_6 & -R_2 & -R_8 & 0 \\ 0 & R_2 & R_1 + R_2 & -R_7 & 0 \\ 0 & -R_8 & 0 & R_5 + R_8 & 0 \\ -R_6 & 0 & 0 & 0 & R_6 + R_7 \end{bmatrix}$$



$$V_1 = i_1 R_1$$


$$V_2 = -i_1 R_1$$

$$V_1 = i_1 (R_1 + R_2)$$

$$V_2 = -i_1 (R_1 + R_2)$$

Sum of all the voltage sources along a loop
 $\int [V_1] - [V_2] =$
 Similarly for other loops

1022013
Q.

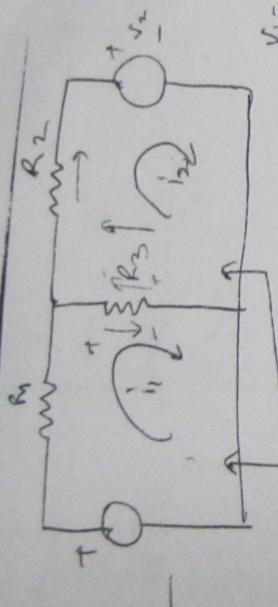

$$\text{Loop eq.: } KVL: V_1 - i_1 R_1 + (i_2 - i_1) R_3 = 0$$

$$i_1 \downarrow i_2 \quad (i_1 - i_2) R_3$$

$$-(i_2 - i_1) R_3 - i_2 R_2 - V_2 = 0,$$

$$(i_1 - i_2) R_3 - i_2 R_2 - V_2 = 0,$$

$$V_1 = i_1 R_1 + (i_1 - i_2) R_3$$

$$V_2 = -(i_2 - i_1) R_3 - i_2 R_2$$

$$V_1 = i_1 (R_1 + R_3) - i_2 R_2$$


$$V_2 = + R_3 i_1 - i_2 (R_2 + R_3)$$

$$-V_2 = -i_1 R_3 + i_2 (R_2 + R_3)$$

$$\text{Sum } \uparrow \text{ and the voltage along the line } \uparrow, \text{ with proper polarity}$$

$$[V_1] = \begin{bmatrix} 1 \\ i_1 \\ -V_2 \end{bmatrix} = \begin{bmatrix} R_1 + R_3 \\ -R_3 \\ R_2 + R_3 \end{bmatrix} \frac{1}{Z}$$

$$[V] = [z][\Sigma]$$

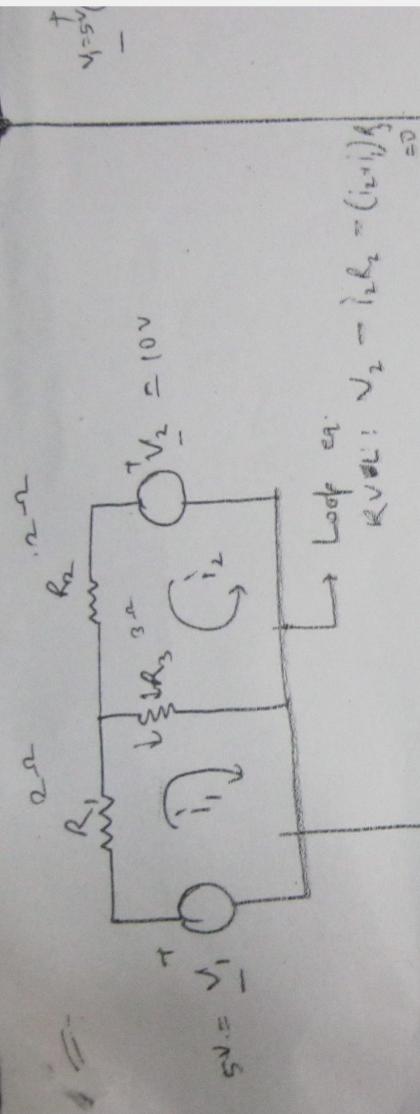

$$KVL: V_1 - i_1 R_1 - (i_1 + i_2) R_3 = 0$$

$$\begin{aligned} V_1 &= i_1 R_1 + (i_1 + i_2) R_3 = i_1 (R_1 + R_3) + i_2 R_3 \\ V_2 &= i_2 R_2 + (i_1 + i_2) R_3 = i_2 R_2 + i_1 (R_3 + R_2) \end{aligned}$$

$$\begin{aligned} 5 - i_1 2 - (i_1 + i_2) 3 &= 0 \\ 10 - i_2 2 - (i_1 + i_2) 3 &= 0 \end{aligned}$$

$$5 - i_1 2 - (i_1 - i_2) 3 = 0$$

$$-(i_2 - i_1) 3 - i_2 2 - 10 = 0$$

$$i_1 = \begin{bmatrix} 5 & -3 \\ -3 & 5 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$i_2 = \begin{bmatrix} 5 & 5 \\ -3 & 10 \end{bmatrix}^{-1} \begin{bmatrix} 35 \\ 16 \end{bmatrix}$$

$$i_1 = \begin{bmatrix} 5 & 3 \\ 3 & 5 \end{bmatrix}^{-1} \begin{bmatrix} 5 \\ 3 \end{bmatrix}$$

$$i_2 = \begin{bmatrix} 5 & 10 \\ 3 & 5 \end{bmatrix}^{-1} \begin{bmatrix} 35 \\ 16 \end{bmatrix}$$