

www.MINEPORTAL.in

(All Mining Solutions)

DOWNLOAD MINEPORTAL APP FROM GOOGLE PLAY STORE

- **ONLINE TEST SERIES FOR**
 - DGMS COAL/METAL FIRST & SECOND CLASS
 - GATE MINING
 - COAL INDIA EXAMS
 - OTHER PSUs MINING EXAMS
- **FREE STUDY MATERIAL-MINEPORTAL NOTES & USER NOTES**
- **MINING VIDEO LECTURES**
- **DISCUSSION FORUM**
- **WHATSAPP CHAT SUPPORT FOR MINING EXAMS & QUERY RELATED TO MINING**

CALL/WHATSAPP- 8804777500

VISITING SITE- www.MINEPORTAL.in

Facebook- www.fb.com/mineportal.in

EMAIL- INFO@MINEPORTAL.IN




IIT(BHU) VARANASI
STUDENTS' NOTES
TOPIC-ELECTRICAL-III

www.MINEPORTAL.in

Shawya

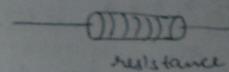
Red \rightarrow 2, Orange \rightarrow 3, Yellow \rightarrow 4, Green \rightarrow 5
 Blue \rightarrow 6, violet \rightarrow 7, grey \rightarrow 8



Q) Find resistances ab and bc

Sol:
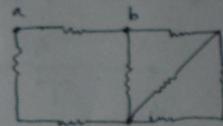
$$\frac{1+3}{2R} \Rightarrow \frac{2R}{3} \parallel R \Rightarrow \frac{5R}{3}$$




$$\frac{\frac{1}{3R} + \frac{1}{R} + \frac{1}{5R}}{\frac{5+15+3}{15R}} \Rightarrow \frac{11R}{27} \quad (bc)$$

$$\frac{\frac{1}{3R} + \frac{1}{R}}{\frac{5R+2R}{8R}} \Rightarrow \frac{3+5}{3R} \times \frac{8R}{8} = \frac{5R}{8}$$


$$\frac{5R+2R}{8R} \Rightarrow \frac{21R}{8}$$
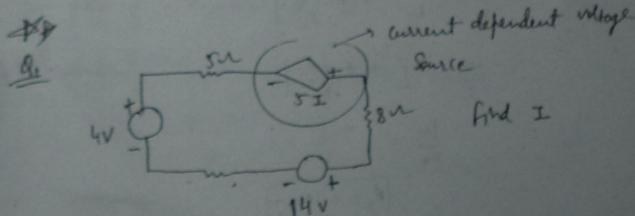
$$\frac{\frac{1}{2R} + \frac{1}{R}}{\frac{2+21}{21R}} \Rightarrow 29 \Rightarrow \frac{21R}{29} \quad (ab)$$



$$\begin{aligned} \text{Sol: } & -46I_1 - 14I_2 - 35I_3 + 4I_4 - 2I_5 = 0 \\ & 10 - 10I_1 = 10 \\ & 14 - 8I_1 - 5I_2 - 5I_3 - 4I_4 - 7I_5 = 0 \quad \boxed{I_1 = -\frac{V}{10} A} \\ & I = \frac{10}{25} \Rightarrow 0.4 \text{ A} \end{aligned}$$

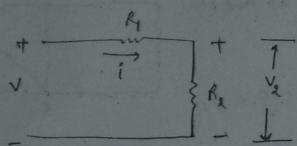Q: In the figure given below, it is desired to get
 $V_2 = \frac{3}{4} V$ find R_2 if $R_1 = 100 \Omega$



$$\text{Sol: } \frac{V - V_2}{R_1} = \frac{0 + V_2}{R_2}$$

$$\frac{V}{R_1} = V_2 \left[\frac{1}{R_1} + \frac{1}{R_2} \right]$$


$$\frac{V}{R_1} = \frac{3}{4} V \left[\frac{1}{R_1} + \frac{1}{R_2} \right]$$

$$\frac{4}{3} = \left[1 + \frac{R_1}{R_2} \right]$$

$$\frac{4}{3} = \left[1 + \frac{100}{R_2} \right]$$

$$\frac{100}{R_2} = +\frac{1}{3}$$

$$\boxed{R_2 = +300 \Omega}$$

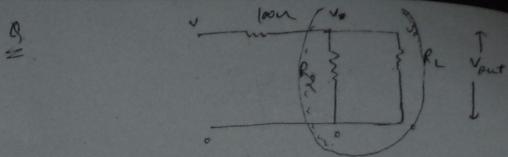

what will be the % change in output voltage if

$$(i) R_L = 10 \text{ k}\Omega \quad (ii) R_L = 1 \text{ k}\Omega$$

$$\text{Sol: } R_2 = 300 \Omega \text{ from previous}$$

$$i = i_1 + i_2$$

$$\frac{V - V_o}{100} = \frac{V_o}{R_2} + \frac{V_o}{R_L}$$

$$\frac{V}{100} = V_o \left[\frac{1}{100} + \frac{1}{R_2} + \frac{1}{R_L} \right] \quad -(i)$$

$$\frac{V}{100} = V_o \left[\frac{1}{100} + \frac{1}{300} + \frac{1}{10000} \right] \quad -(i)$$


$$\frac{V}{100} = V_o \left[\frac{1}{100} + \frac{1}{300} + \frac{1}{10000} \right]$$

$$\frac{V_o - V_{o1}}{V_o} \Rightarrow 1 - \frac{V_{o1}}{V_o}$$

$$\Rightarrow 1 - \frac{\left[\frac{1}{100} + \frac{1}{300} + \frac{1}{10000} \right]}{\left[\frac{1}{100} + \frac{1}{300} + \frac{1}{10000} \right]}$$

$$\Rightarrow \frac{\frac{1}{100} - \frac{1}{10000}}{\left(\frac{1}{100} + \frac{1}{300} + \frac{1}{10000} \right)} = \frac{9 \times 10^{-4} \times 10^{-4}}{0.041} = \frac{9 \times 10^{-8}}{0.041} = \frac{9 \times 10^{-8}}{4.1} = 2.19 \%$$

Q. Find v_1 and i_2

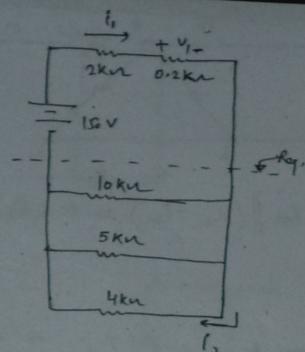

$$S.t. \frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{5} + \frac{1}{4} = 0.55 \Rightarrow 1.82 \text{ k}\Omega = R_{eq}$$

$$\text{Current } i_1 = \frac{150 \text{ volt}}{2\text{k}\Omega + 0.2\text{k}\Omega + 1.82\text{k}\Omega} \\ = \frac{150}{4.02\text{k}\Omega} = 37.3 \text{ mA}$$

$$V_1 = 0.2\text{k}\Omega \times i_1 = 0.2\text{k}\Omega \times 37.3 \text{ mA} = 32.3 \times 0.2 \text{ V} \\ = 7.46 \text{ V}$$

$$\text{Voltage across } R_{eq} = R_{eq} \times i_1 = 1.82 \text{ k}\Omega \times 37.3 \text{ mA} \\ = 67.886 \text{ volt}$$

$$\text{Current through } 4\text{k}\Omega = \frac{\text{Voltage across } 4\text{k}\Omega}{4\text{k}\Omega} \\ = \frac{67.886 \text{ V}}{4\text{k}\Omega} \\ = 16.97 \text{ mA}$$

Ans of previous question.


(i) when $R_L = 10\text{k}\Omega$

$$V_L = \frac{R_L}{R_1 + R_L} V \\ = \frac{291.26}{10 + 291.26} \text{ V} = \frac{291.26}{301.26} \text{ V} \\ = 0.744$$

$$\frac{0.744 - 0.744}{0.75} \times 100 \quad \underline{i_2}$$

(ii) when $R_L = 1\text{k}\Omega$

Q. f - Δ Conversion, star - Δ conversion

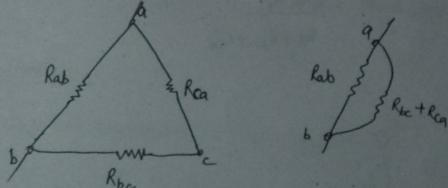

$$\text{for pair of nodes ab } R_a + R_b = R_{ab} \parallel (R_{bc} + R_{ca}) \quad \text{---(1)}$$

$$\text{for bc } \text{Similarly } R_b + R_c = R_{bc} \parallel (R_{ca} + R_{ab}) \quad \text{---(2)}$$

for ca

$$R_c + R_a = R_{ca} \parallel (R_{ab} + R_{bc}) \quad \text{---(3)}$$

Moving eqn (1), (2), (3)

$$R_{ab} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

Similarly

$$R_{bc} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

$$R_{ca} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

and

$$R_a = \frac{R_{ab} R_{ac}}{R_{ab} + R_{ac} + R_{bc}}$$



Similarly

$$R_b = \frac{R_{ba} R_{bc}}{R_{ab} + R_{bc} + R_{ca}}$$


$$R_c = \frac{R_{ca} R_{cb}}{R_{ab} + R_{bc} + R_{ca}}$$

$\gamma - \Delta$ conversion
Star-delta conversion

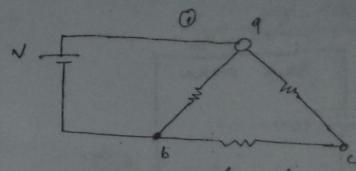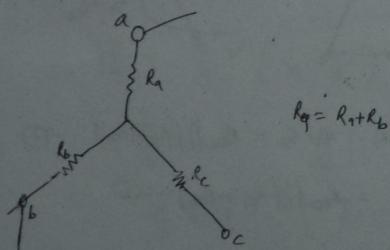
$\Delta - Y$ conversion
Delta-star conversion


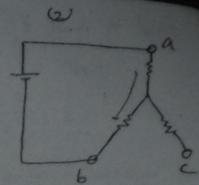
$$R_{ab} \parallel (R_{bc} + R_{ca}) = R_a + R_b$$




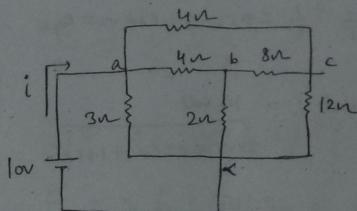
Q. Find current i using $\gamma - \Delta$ or $\Delta - \gamma$ conversion.



Sol:


Star-delta conversion

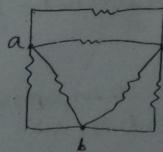

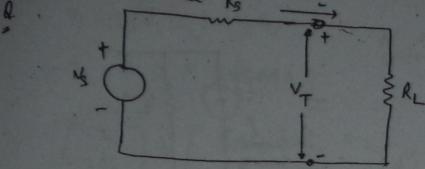

Practical voltage source

$$V_T = \frac{V_s}{R_s + R_L} R_L$$

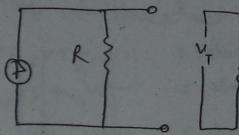

$$KVL \rightarrow V_T = V_s - I_L R_s \leftarrow V-I characteristic$$

$$I_L R_s + V_T = V_s$$



$$I_L R_s = V_s - V_T \Rightarrow y = mx + c$$

$$KCL \rightarrow I_L = \frac{V_s}{R_s} - \frac{V_T}{R_s}$$


$$y \quad c \quad x$$

$$= \left(-\frac{1}{R_s} \right) V_T + \frac{V_s}{R_s} \rightarrow V_T - I_L \text{ characteristic}$$

$$m = -\frac{1}{R_s}$$

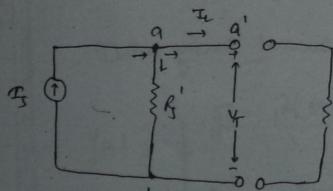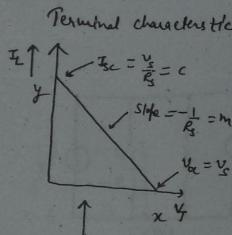

Practical current source

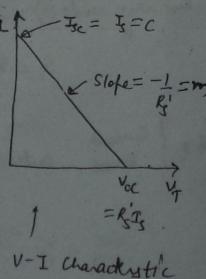

V-I characteristic

$$KCL \text{ at node } a \quad I_s = \frac{V_T}{R_s} + I_L$$

$$I_L = -\frac{1}{R_s} V_T + I_s$$

$$y = mx + c$$

I_{sc} = short circuit current (when $y=0$)

V_{oc} = open circuit voltage (when $I_L=0$)

Comparing eqn ① and ②

$$R_s' = R_s$$

$$V_s = I_s R_s = V_{oc} \rightarrow \text{source terminal pair}$$


$$R_s' = \frac{V_s}{I_s} = I_{sc} \rightarrow \text{short circuit current}$$

current through zero
resistance load connected
source terminals,

Nodal analysis:-

Basic electrical engineering → I-T. Nagrath

①



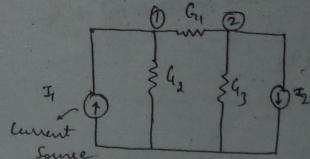


$$G_1 = \frac{1}{R_s} = \text{conductance}$$

KCL

Node 1:

Node 2:

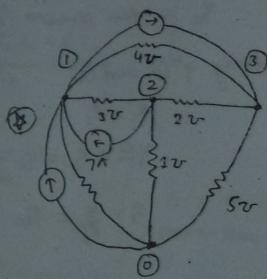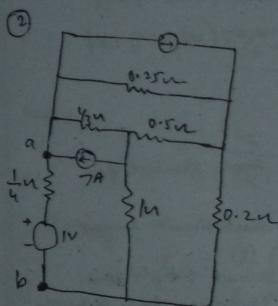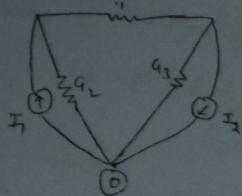

$$\frac{V_1 - V_2}{G_2} \neq$$

Current from ① to ② = Current from ② to ③ + I_2

$$\text{node ① } I_1 = (V_1 - V_2) G_1 + V_2 G_2 \\ (V_1 - V_2) G_1 = V_2 G_2 + I_2$$

Given $i_1 = 2A, i_2 = -3A$

$$G_1 = 0.2\Omega; G_2 = 1\Omega; G_3 = 0.5\Omega$$

$V_1 = ?$

$V_2 = ?$



$$\text{S1:2}$$

$$= \frac{V_1}{1\Omega} = 4A \quad (V_1 = 4V)$$

$$V = IR \quad I = \frac{V}{R} = \frac{V_1}{1\Omega} = 4A$$

$$\begin{aligned} \text{node 1: } & 1V_1 - 3V_2 - 4V_3 = 5 \\ \text{node 2: } & -3V_1 + 6V_2 - 2V_3 = -7 \\ \text{node 3: } & -4V_1 - 2V_2 + 11V_3 = 6 \end{aligned}$$

Later

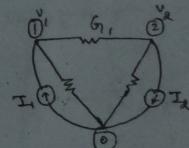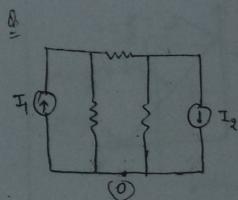

datum node
or kcl
At node ①

datum node
or
reference node

entering node ① = sum of current leaving node ①

$$I_1 = V_2 G_2 + (V_1 - V_2) G_1 - \textcircled{1}$$

kcl
at node ②

entering node ② = sum of current leaving node ②

$$-I_2 = V_3 G_3 + (V_2 - V_3) G_2 - \textcircled{2}$$

$$I_1 = v_1(G_{23} + G_3) - v_2 G_1$$

$$-I_2 = -v_1 G_1 + v_2 (G_{13} + G_3)$$

$$\begin{bmatrix} I_1 \\ -I_2 \end{bmatrix} = \begin{bmatrix} G_{12} + G_2 & G_1 \\ -G_1 & G_1 + G_3 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

from previous

$$\begin{bmatrix} 5 \\ -7 \\ 6 \end{bmatrix} = \begin{bmatrix} 11 & -3 & -4 \\ -3 & 6 & -2 \\ 4 & -8 & 11 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

** node admittance matrix

$$G^T I = G^T G V$$

$$G^T I = V$$

Cramer's rule:

$$V_1 = \frac{\begin{vmatrix} 5 & -3 & -4 \\ -7 & 6 & -9 \\ 6 & -2 & 11 \end{vmatrix}}{|G|}$$

$$\Rightarrow \frac{115 + 88}{|G|}$$

$$\Rightarrow \frac{203}{|G|}$$

$$\Rightarrow 4.62$$

$$|G| = \begin{vmatrix} 11 & -3 & -4 \\ -3 & 6 & -2 \\ 4 & -8 & 11 \end{vmatrix}$$

$$= 439$$

$$\Rightarrow V_1 = \frac{203}{439} = 0.462$$

$$V_2 = \frac{\begin{vmatrix} 11 & 5 & -2 \\ -3 & 6 & 11 \\ -4 & -8 & 11 \end{vmatrix}}{|G|} = -0.743$$


$$V_3 = 0.579$$

conductance

$$G = \frac{1}{R} \rightarrow \text{Resistance}$$

$$Y = \frac{1}{R + jX} \rightarrow \text{Impedance}$$

admittance

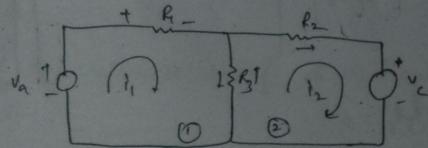

$$KVL(1) : V_a - R_1 i_1 - R_3 (i_1 - i_2) - V_b = 0$$

$$KVL(2) : V_b - R_3 (i_2 - i_1) - R_2 i_2 - V_c = 0$$


$$-R_1 i_1 - R_3 (i_1 - i_2) = V_b - V_a$$

$$+ R_3 (i_2 - i_1) + R_2 i_2 = V_b - V_c \quad \text{--- (2)}$$

$$R_1 i_1 + R_3 (i_1 - i_2) = V_a - V_b \quad \text{--- (1)}$$

$$\begin{bmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_a - V_b \\ V_b - V_c \end{bmatrix}$$

Q2

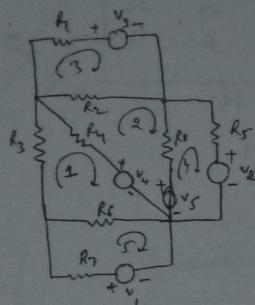

$$St \quad V_{n \times 1} = Z_{n \times n} \times I_{n \times 1}$$

$$\begin{bmatrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \end{bmatrix} = \begin{bmatrix} -v_4 \\ v_4 - v_5 \\ -v_3 \\ v_5 - v_2 \\ v_1 \end{bmatrix} = \begin{bmatrix} \\ \\ \\ \\ \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{bmatrix}$$

$$v_r - i_5 R_7 - i_5 R_6 = 0$$

$$-R_2 i_4 - R_3 i_1 - R_4 (i_1 - i_2) v_1 = 0 \quad - R_6 (i_1 - i_5) = 0$$

~~$$-R_2 i_2 + v_4 - R_4 (i_2 - i_1) - (i_2 R_8 - v_5) = 0$$~~

$$-i_4 R_5 - v_2 + v_5 - R_8 (i_4 - i_2) = 0$$

$$-i_3 R_4 - v_3 - R_2 (i_3 - i_2) = 0$$